



145 MHz 40W power amplifier based on the Hybrid Module Mitsubishi M57727

Matthias, DD1US, January 19th 2020, rev 1.0


Recently I bought a power amplifier at a Ham Radio flea-market. It is based on a hybrid module M57727 from Mitsubishi. Based on the low price I assumed that the module itself is defective but that I could use the PCB and heatsink and mount other modules with the same pinout on to it.


The PCB seems to be cut out from a larger PCB and has some callsigns printed on it. Based on this I was able to identify the PCB being part of a 144 MHz linear transverter with an IF frequency of 28 MHz. It was published in 1999 by F5FLN, F4ARU and F4ARY in the French journal Reunion THF Francaise Cj99.

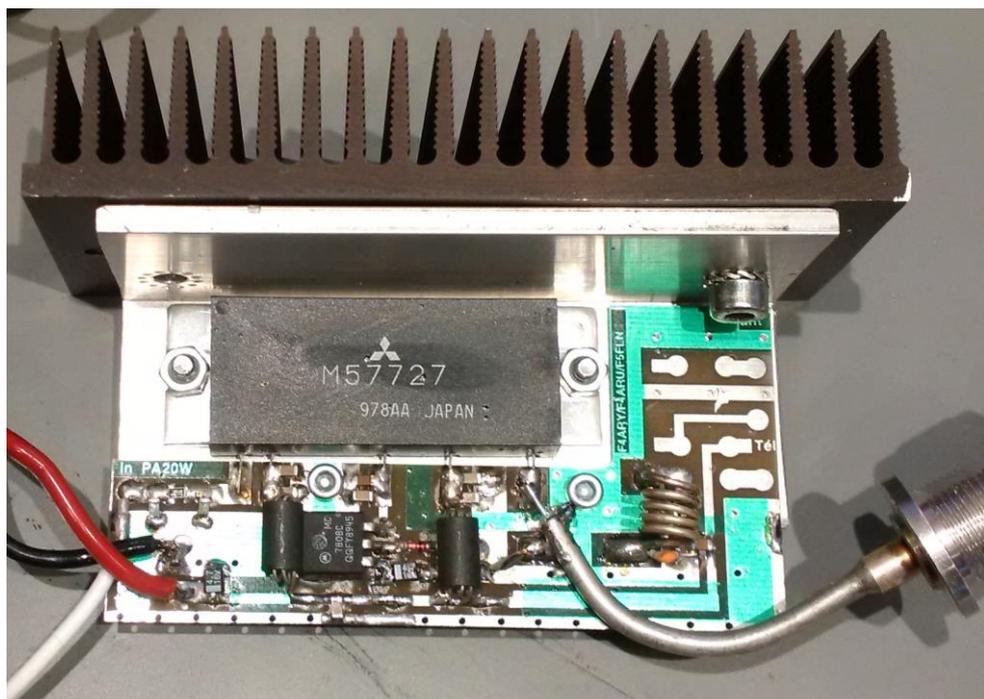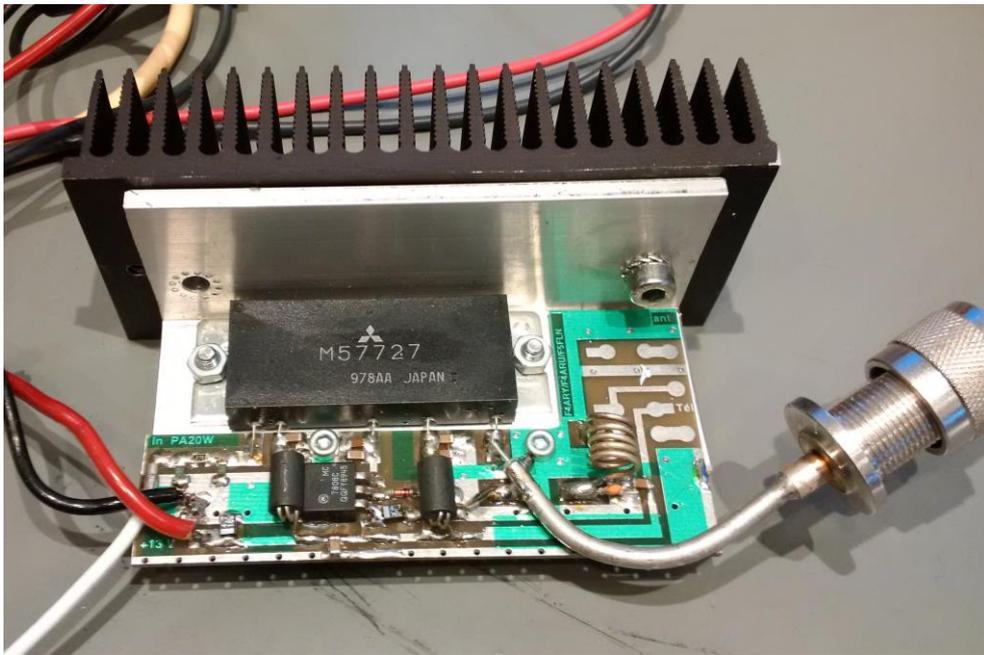Here are pictures of the power amplifier:



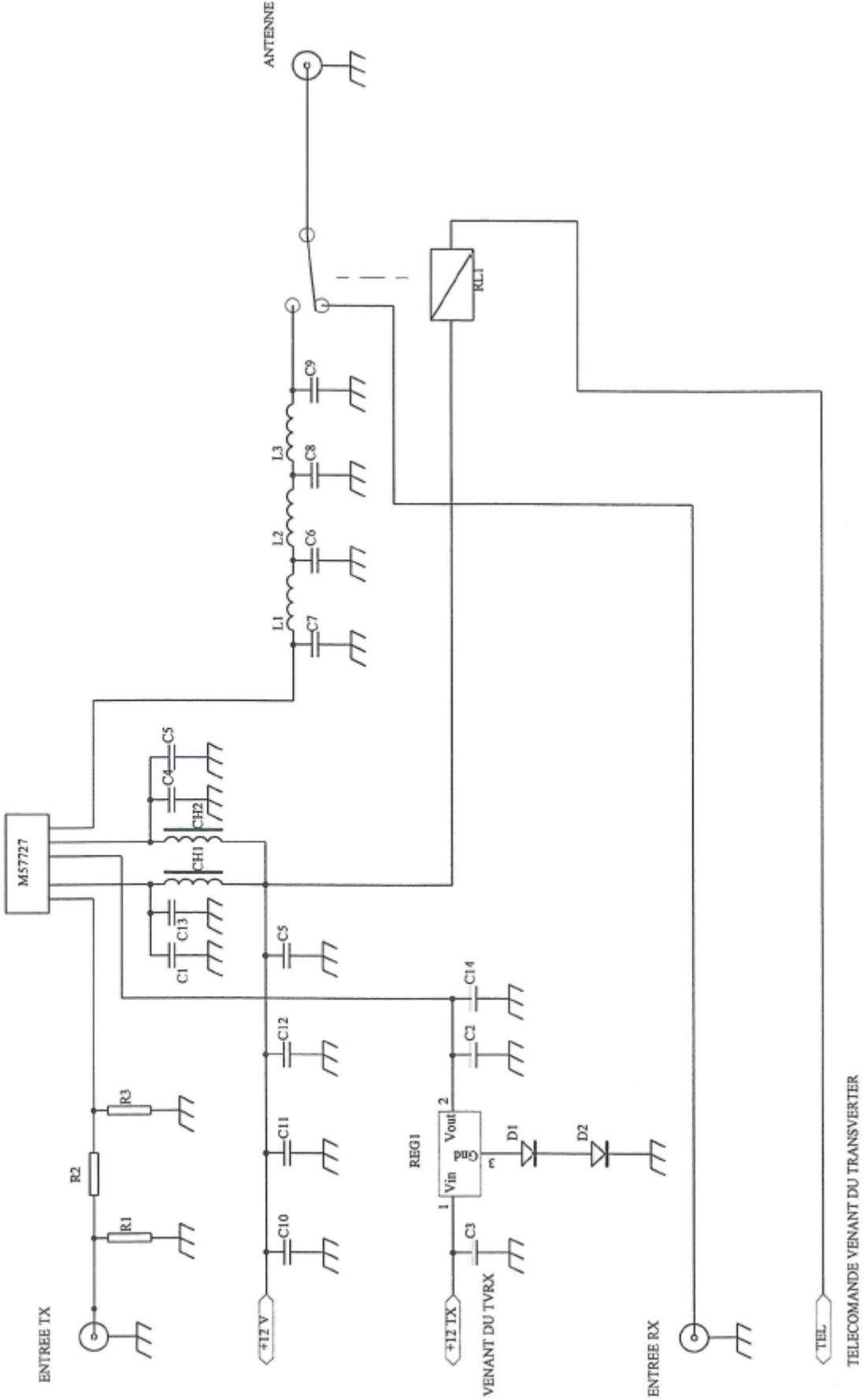Here is the information I found in the Journal Cj99:



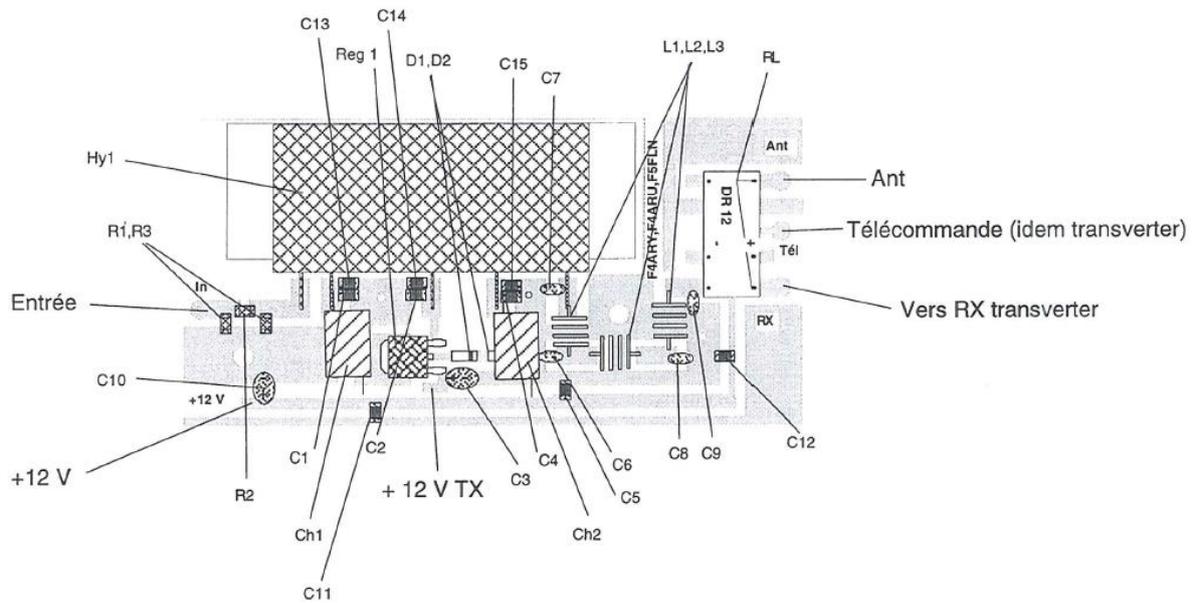

NOMENCLATURE AMPLI 20W

| N° | REPERE | DESIGNATION | FOURNISSEUR | OBSERVATIONS |
|----|--------|-------------|-------------|--------------------|
| 1 | C1 | 1nF | CHOLET | CMS |
| 2 | C2 | 1nF | CHOLET | CMS |
| 3 | C3 | 4,7µF 25V | CHOLET | CMS |
| 4 | C4 | 1nF | CHOLET | CMS |
| 5 | C5 | 100nF | CHOLET | CMS |
| 6 | C6 | 39pF | CHOLET | CAPA NPO céramique |
| 7 | C7 | 18pF | CHOLET | CAPA NPO céramique |
| 8 | C8 | 39pF | CHOLET | CAPA NPO céramique |
| 9 | C9 | 18pF | CHOLET | CAPA NPO céramique |
| 10 | C10 | 4,7µF 25V | CHOLET | CMS |
| 11 | C11 | 100nF | CHOLET | CMS |
| 12 | C12 | 100nF | CHOLET | CMS |
| 13 | C13 | 100nF | CHOLET | CMS |
| 14 | C14 | 100nF | CHOLET | CMS |
| 15 | C15 | 100nF | CHOLET | CMS |
| 16 | | | | |
| 17 | L1 | 5 TOURS | 10/10 AG | ∅ 6 |
| 18 | L2 | 5 TOURS | 10/10 AG | ∅ 6 |
| 19 | L3 | 5 TOURS | 10/10 AG | ∅ 6 |
| 20 | CH1 | VK200 | CHOLET | |
| 21 | CH2 | VK200 | CHOLET | |
| 22 | R1 | 150Ω | CHOLET | CMS |
| 23 | R2 | 27Ω | CHOLET | CMS |
| 24 | R3 | 150Ω | CHOLET | CMS |
| 25 | REG1 | 78M08 | CHOLET | CMS |
| 26 | D1 | PMLL4153 | CHOLET | 1N4148 CMS |
| 27 | D2 | PMLL4153 | CHOLET | 1N4148 CMS |
| 28 | HY1 | M57527 | CHOLET | |
| 29 | RL | DR12 | CHOLET | |


When I got from the flea-market I started refurbish the amplifier in order to be able to test it. The output filter was not assembled and I decided to test the power amplifier module without any external output matching.

Based on the datasheet of the M57727 module this amplifier should be capable to deliver up 37W on 145 MHz. The supply voltages are V1=12.5V, V2=9V and V3=12.5V.


Here is a copy of the datasheet:

TYPICAL PERFORMANCE DATA

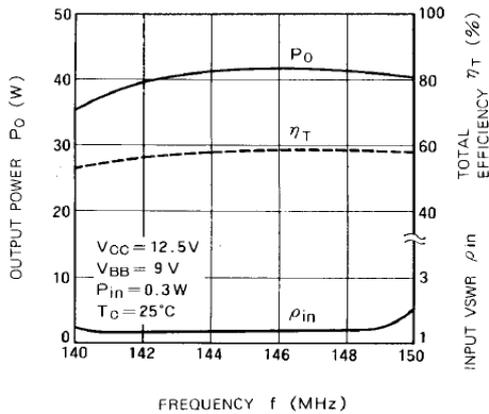
OUTPUT POWER, TOTAL EFFICIENCY, INPUT VSWR VS. FREQUENCY




POWER GAIN VS. FREQUENCY

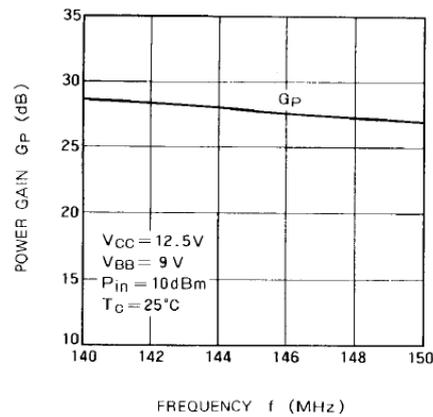

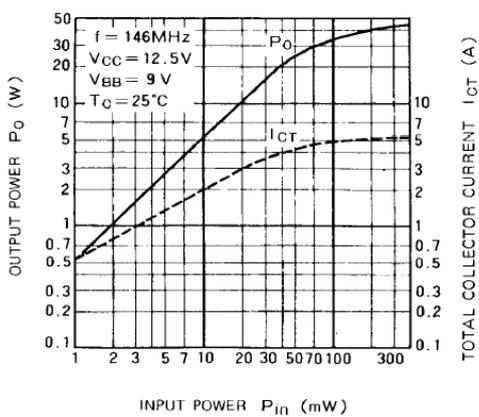OUTPUT POWER, TOTAL COLLECTOR CURRENT VS. INPUT POWER



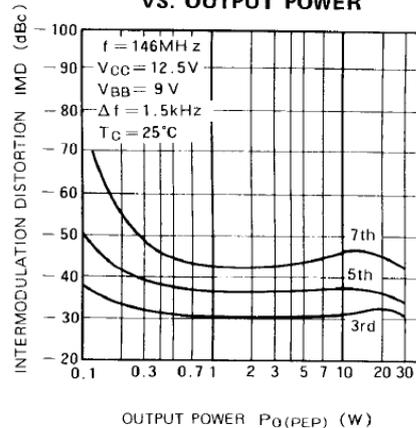INTERMODULATION DISTORTION VS. OUTPUT POWER




I measured the output power as a function of the drive level. I operated the PA at a supply voltage of 12.5V. The quiescent current is 540mA.

The small signal gain is 22.4dB dropping to a value of 21.7dB over a wide input power range before hitting the P1dB which is +43.5dBm or 22W. The drain efficiency at P1dB is approx..35%. Increasing the input power further and driving the amplifier into saturation increases the drain efficiency up to 52.6% at an output power of 46dBm or 40W.

I was surprised that the hybrid module seems to be perfectly ok meeting the specifications from Mitsubishi spot on.

Here are the measurement results:

Pout, Gain and Is versus Pin @145MHz

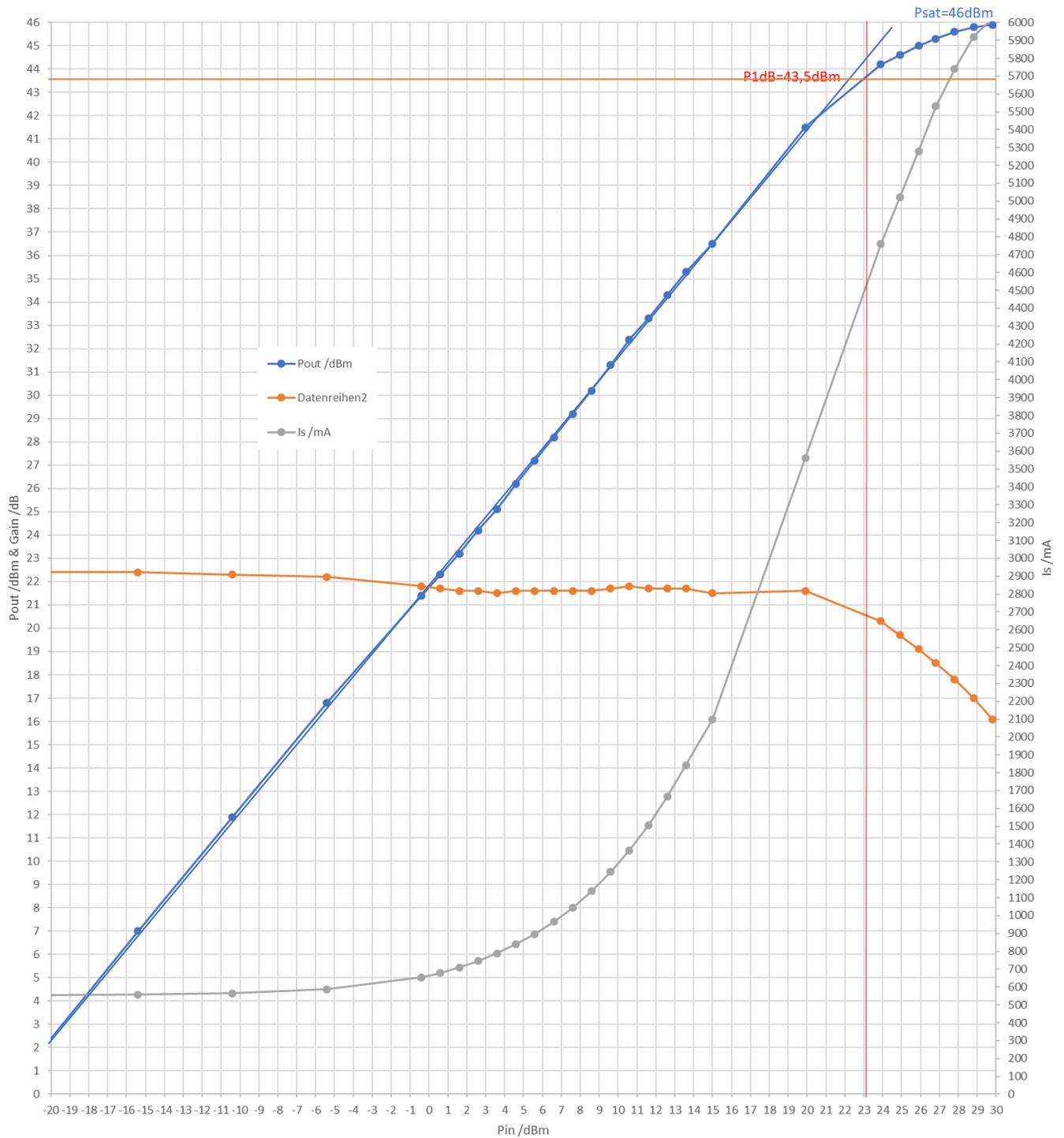

I am always grateful to get feedback and will be happy to answer questions.

Please direct them to the Email address which you will find below.

Best regards

Matthias DD1US

Email: DD1US@AMSAT.ORG

Homepage: <http://www.dd1us.de>